

Measurement Systems


Tadeusz Stepinski, Signaler och system

□ Elements of measurement systems

- ⇒ Bridge circuits
- ⇒ Analogue function circuits
 - > differential amplifier
 - > summing amplifiers
 - > logarithmic amplifier
- ⇒ Analog filters

1

Bridge Configurations

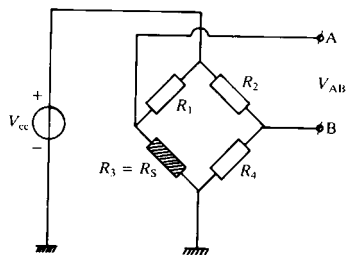

□ One sensor element

- > Bridge as a compensator
- > Bridge as a basic circuit for measuring passive variables
- > Absolute measurement of resistance deviation

$$R_1 = R_2 = R_4 = R \quad R_3 = R(1 + \delta)$$


$$V_{AB} = V_{CC} \left[\frac{R(1 + \delta)}{R + R(1 + \delta)} - \frac{R}{2R} \right]$$

$$V_{AB} = V_{CC} \frac{\delta}{4 + 2\delta} \approx V_{CC} \frac{\delta}{4}$$

Nonlinear effect

2

Bridge Configurations

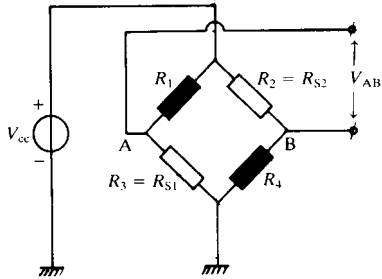

- Two sensor elements
 - > Differential measurement of resistance deviation
 - > High amplification
 - > Used for temperature compensation

$$R_1 = R_4 = R \quad R_2 = R_3 = R(1 + \delta)$$


$$V_{AB} = V_{CC} \left[\frac{R(1 + \delta)}{R(2 + \delta)} - \frac{R}{R(2 + \delta)} \right]$$

$$V_{AB} = V_{CC} \frac{\delta}{2 + \delta} \approx V_{CC} \frac{\delta}{2}$$

Nonlinear effect

3


Bridge Configurations

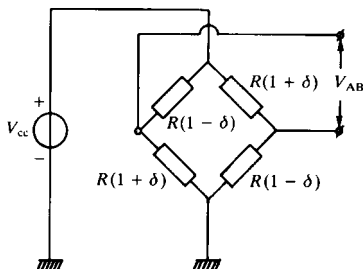

- Four sensor elements
 - > Differential measurement of resistance deviation
 - > Very high gain

$$V_{AB} = V_{CC} \delta$$

- > Example:
 - strain gauge

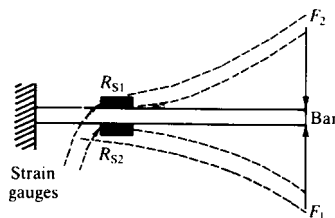


4


Bridge Amplifier Configurations



□ Bridge with differential amplifier

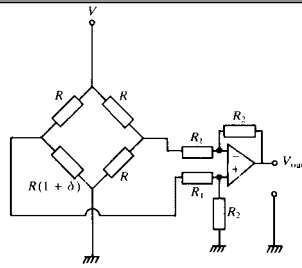

> one sensor element

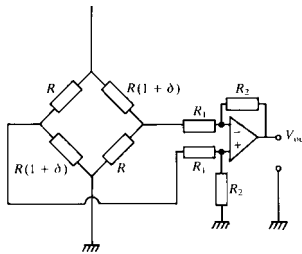


> two sensor elements

Bridge Amplifier Configurations




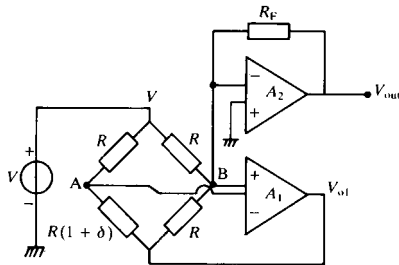□ Linearized configuration of a bridge with one sensor in feedback



$$V_{out} = (R_f / R) V \delta$$

Amplifier Configurations

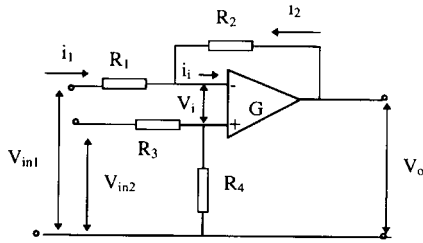

□ Differential operational amplifier


$$V_o = \left(1 + \frac{R_2}{R_1}\right) \frac{R_4}{R_3 + R_4} V_{in2} - \frac{R_2}{R_1} V_{in1}$$

if $R_1 = R_3$ and $R_2 = R_4$

$$V_o = \frac{R_2}{R_1} (V_{in2} - V_{in1})$$

7

Amplifier Configurations

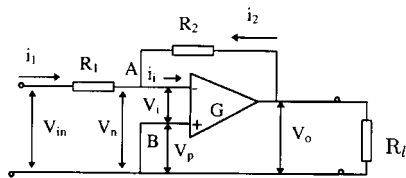


□ Operational amplifiers with feedback loop

> ordinary amplifier

$$V_{out} = (-R_2 / R_1) V_{in}$$

> fractional feedback

> high gain for low resistor values

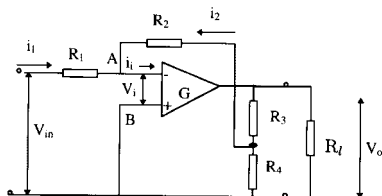


$$V_{out} = - [(R_3 + R_4) / R_4] (R_2 / R_1) V_{in}$$


8

Instrumentation Amplifier

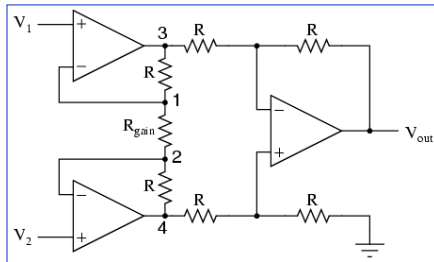- An amplifier with two symmetrical inputs
 - =High impedance at both inputs
 - =High rejection ratio of common mode signals



Principal schema

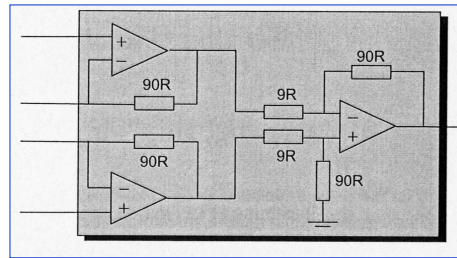


Example of an integrated amplifier

9

Instrumentation Amplifier - CMRR

- Common Mode Rejection Ratio (CMRR)

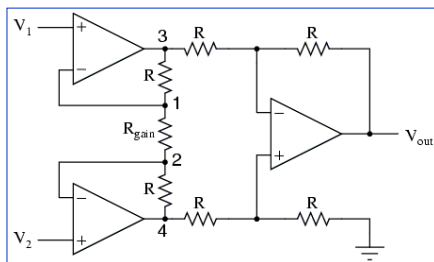

$$V_{out} = K_{NM} V_{NM} + K_{CM} V_{CM}$$

$$V_{NM} = V_2 - V_1$$

$$V_{CM} = (V_2 + V_1)/2$$

K_{NM} - normal mode gain

K_{CM} - common mode gain


$$CMRR = 20 \log \frac{K_{NM}}{K_{CM}}$$

Example: thermoelement

1

0

Amplifier Configurations

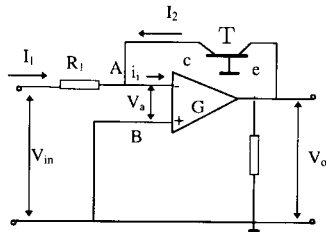

□ Logarithmic amplifier

for the transistor

$$I_C = I_{SS} \exp(qV_{BE}/kT)$$

where: I_{SS} saturation current
for node A


$$\frac{V_{in}}{R_1} + I_C = 0 \quad \text{and} \quad \frac{V_{in}}{R_1} + I_{SS} \exp\left(\frac{qV_o}{kT}\right) = 0$$

since $V_{BE} = V_o$

$$V_o = -\frac{kT}{q} \ln\left(\frac{V_{in}}{R_1 I_{SS}}\right)$$


□ Exponential expansion

$$V_o = R_1 I_{SS} \exp(qV_{in}/kT)$$

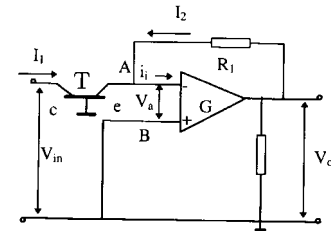

1
1

Amplifier Configurations

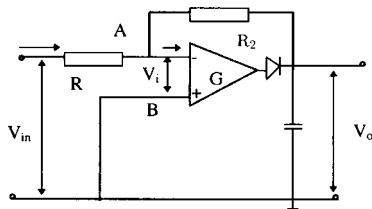

□ Peak detector


1
2

Filter Configurations

□ Second order low pass filter with variable gain

$$\frac{E_o(s)}{E_i(s)} = \frac{K\omega_o^2}{s^2 + s\omega_o/Q + \omega_o^2}$$
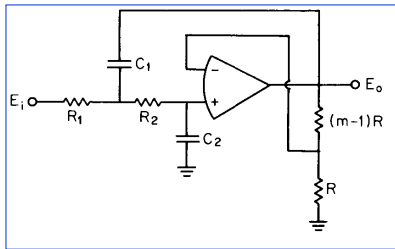
$$\frac{E_o(s)}{E_i(s)} = \frac{m/(R_1R_2C_1C_2)}{s^2 + s [1/R_1C_1 + 1/R_2C_1 - (m-1)/R_2C_2] + 1/R_1R_2C_1C_2}$$



$$K\omega_o^2 = \frac{m}{R_1R_2C_1C_2}$$

$$\frac{\omega_o}{Q} = \frac{1}{R_1C_1} + \frac{1}{R_2C_1} - \frac{m-1}{R_2C_2}$$

$$\omega_o^2 = \frac{1}{R_1R_2C_1C_2}$$

1


3

Filter Configurations

□ Second order high pass filter with variable gain

$$\frac{E_o(s)}{E_i(s)} = \frac{Ks^2}{s^2 + s\omega_o/Q + \omega_o^2}$$
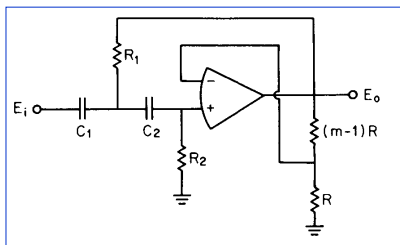
$$\frac{E_o(s)}{E_i(s)} = \frac{s^2m}{s^2 + s [1/R_2C_2 + 1/R_2C_1 - (m-1)/R_1C_1] + 1/R_1R_2C_1C_2}$$



$$K = m$$

$$\omega_o^2 = \frac{1}{R_1R_2C_1C_2}$$

$$\frac{\omega_o}{Q} = \frac{1}{R_2C_2} + \frac{1}{R_2C_1} - \frac{m-1}{R_1C_1}$$

1

4

Filter Configurations

□ Second order universal active filter

$$\frac{E_L(s)}{E_i(s)} = \frac{K_L \omega_o^2}{s^2 + s\omega_o/Q + \omega_o^2} \quad \text{low-pass}$$

$$\frac{E_H(s)}{E_i(s)} = \frac{K_H s^2}{s^2 + s\omega_o/Q + \omega_o^2} \quad \text{high-pass}$$

and

$$\frac{E_B(s)}{E_i(s)} = \frac{K_B s\omega_o/Q}{s^2 + s\omega_o/Q + \omega_o^2} \quad \text{bandpass}$$


where $\omega_o = \sqrt{\frac{K_3}{R_1 R_2 C_1 C_2}}$

$$Q = \frac{1 + K_4}{1 + K_3} \sqrt{\frac{K_3 R_1 C_1}{R_2 C_2}}$$

$$K_L = \frac{K_4(1 + K_3)}{K_3(1 + K_4)}$$

$$K_H = \frac{K_4(1 + K_3)}{1 + K_4}$$

$$K_B = -K_4$$

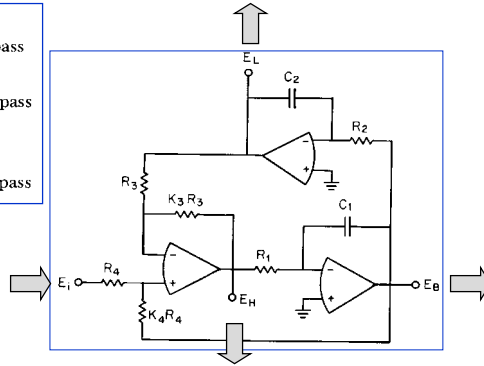

□ Two integrators and one summing amplifier - state variable technique


1

5

Filter Configurations

□ Band rejection filter using the state variable technique
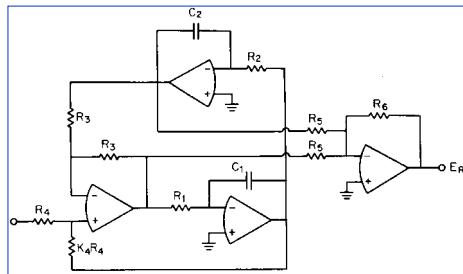
$$\frac{E_R(s)}{E_i(s)} = \frac{K_R(s^2 + \omega_o^2)}{s^2 + s\omega_o/Q + \omega_o^2}$$



□ Additional summing amplifier - sum of LP and HP

1

6